

④

Current loop design.

a) Find $P_{elec}(s) = \frac{V_s(s)}{V_c(s)}$ with the back emf voltage

we have.

$$V_s = (I_c \times R_s) \frac{25K}{5K} = 5(I_c \times R_s)$$

$$V_s = I_c \quad (1)$$

$$\begin{cases} V_a = K_f \dot{x} + (Z_{Lc} + R_c + R_s) I_c \\ 5V_c = V_a \end{cases}$$

$$\Rightarrow \begin{cases} 5V_c = K_f \dot{x} + V_s (Z_{Lc} + R_c + R_s) \\ 5V_c = V_a \\ V_s = I_c \end{cases} \quad (2)$$

Also from the mechanic system we have:

$$f - m_1 \ddot{x} - K_1 x - b_1 \dot{x} = 0$$

$$\Rightarrow f = m_1 \ddot{x} + K_1 x + b_1 \dot{x}$$

$$\Rightarrow K_f I_c(s) = m s^2 X(s) + K_1 X(s) + b_1 s X(s)$$

$$\Rightarrow X(s) = \frac{K_f I_c(s)}{m s^2 + K_1 + b_1 s} \quad (3)$$

(3) \rightarrow (2) we have.

$$5V_c = K_f s X(s) + (sL + R_c + R_s) I_c$$

$$\Rightarrow 5V_c = \frac{K_f s I_c K_f}{m_1 s^2 + K_1 + b_1 s} + V_s (sL + R_c + R_s)$$

$$\Rightarrow \frac{V_s}{V_c} = \frac{5(m_1 s^2 + b_1 s + K_1)}{K_f^2 s + (sL + R_c + R_s)(m_1 s^2 + K_1 + b_1 s)}$$

4 (b) $P_{clcr}(s) = \frac{V_s(s)}{V_c(s)}$ without emf.

$$5V_c = V_a$$

$$\begin{cases} V_a = I_c (Z_L + R_c + R_s) \\ V_s = 3I_c \end{cases} \Rightarrow \boxed{\frac{V_s(s)}{V_c(s)} = \frac{5}{sL + R_c + R_s}}$$

(c) at high frequency we have.

$$\frac{V_s(s)}{V_c(s)} \approx \frac{5(m_1 s^2 + b_1 s + K_1)}{(sL + R_s + R_c)(m_1 s^2 + b_1 s + K_1)} = \boxed{\frac{5}{sL + R_c + R_s}}$$

which is equal to the each other

(d) Node Voltage:

$$\frac{0 - V_{set}}{R_1} + \frac{0 - I_c (Z_L + R_s + R_c)}{5R_{eq}} - \frac{0 - V_s}{R_2} = 0$$

$$\Rightarrow \frac{V_{set}}{R_1} = -I_c \left(\frac{Z_L + R_s + R_c}{5R_{eq}} + \frac{1}{R_2} \right)$$

$$\Rightarrow \frac{I_c}{V_{set}} = \frac{-5R_{eq}R_2}{R_1R_2(Z_L + R_s + R_c) + 5R_1R_{eq}}$$

$$\Rightarrow \boxed{\frac{I_c}{V_{set}} = \frac{-5(R_3 s C_1 + 1)R_2}{R_1R_2(sL + R_s + R_c)s(R_3 s C_2 + C_2 + C_1) + 5R_1(R_3 s C_1 + 1)}}$$

$$\Rightarrow \left. \frac{I_c}{V_{set}} \right|_{s=0} = -0.5 \Rightarrow -0.5 = \frac{-R_2}{R_1} \Rightarrow \boxed{R_2 = \frac{1}{2}R_1 = 5K}$$

$s = \left(\frac{1}{T}\right)$

$$\text{Set } V_s = 0$$

$$\Rightarrow \frac{0 - V_c}{R_{eq}} + \frac{0 - V_s}{R_2} \Rightarrow \frac{-V_c(s)}{V_s(s)} = \frac{R_{eq}}{R_2} = \frac{R_3 s C_2 + 1}{[s(R_3 s C_2 + C_2 + C_1)]} R_2$$


4

d) unity - lead compensator

$$C_{lead}(s) = K \frac{1 + \alpha T s}{2(1 + T s)}$$

$$\frac{-V_c(s)}{V_s(s)} = \frac{R_3 C_2 \left(s + \frac{1}{R_3 C_2} \right)}{s R_2 \left(R_3 C_2 \left(s + \frac{1+C_2}{R_3 C_2 C_1} \right) \right)}$$
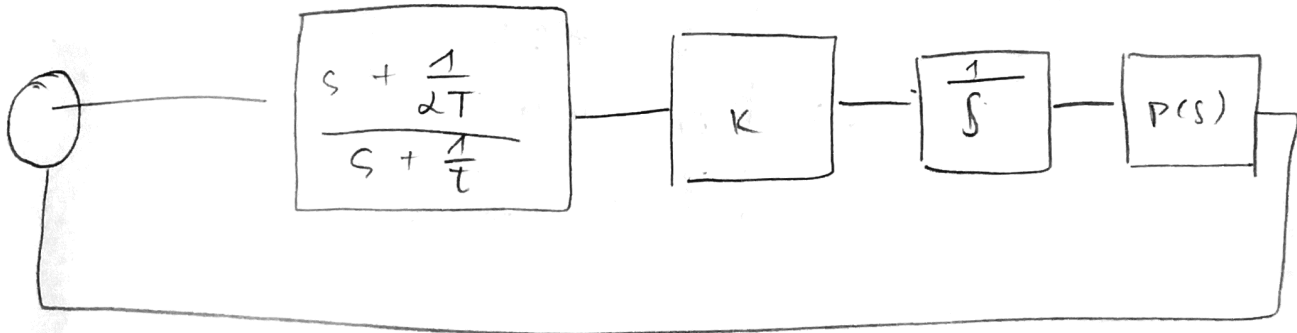
$$= \frac{R_3 C_2 \left(s + \frac{1}{R_3 C_2} \right)}{s R_2 (1+C_2) \left(\frac{R_3 C_2 C_1}{1+C_2} s + 1 \right)} = \frac{s + \frac{1}{R_3 C_2}}{(s R_2)(1+C_2) \left(s + \frac{1+C_2}{R_3 C_2 C_1} \right)}$$



Plot and looking at the $\frac{1}{s} P(s)$ we have. Phase angle at $\omega = 6 \times 10^5 \text{ rad/s}$

$$\Rightarrow \phi_m = 60^\circ - (180^\circ - 118^\circ) =$$

$$\Rightarrow \alpha = \frac{1 + \sin 58^\circ}{1 - \sin 58^\circ} = 12.16$$

$$\Rightarrow \alpha T = 6.9 \times 10^{-6}$$

$$\Rightarrow T = \frac{1}{\omega \sqrt{\alpha}} = \frac{1}{6 \times 10^5 \times \sqrt{12.16}} = 4.77 \times 10^{-7}$$

$$\Rightarrow \left| K_{lead} \left(\frac{1 + \alpha T s}{2(1 + T s)} \right) \left(\frac{s}{L_c s + R_s + R_c} \right) \right| = 1$$

④ \Rightarrow

$$\left| K_{rad} \frac{1 + 5.7 \times 10^{-6} s}{12.16 + 5.7 \times 10^{-6} s} \times \left(\frac{s}{2 \times 10^{-4} s + 4.2} \right) \right| = 1$$

$$\Rightarrow K_{rad} = 2.432$$

We use all the parameters and plot the transfer function, we can see that, it did not satisfy the requirement, so we changed K_{rad} by increasing it and some trial experiments, we got:

$$K_{rad} = 5,000,000 \Rightarrow \frac{1}{R_2 C_1} = 5,000,000$$

$$\Rightarrow C_1 = 4 \times 10^{-11} \text{ F}$$

$$\frac{1}{R_3 C_2} = 2.6 \times 10^{-5}$$

\Rightarrow

$$\frac{C_1 + C_2}{R_3 C_2 C_1} = 2.86 \times 10^{-6}$$

$$\begin{aligned} R_3 &= 125 \text{ K} \\ C_1 &= 4 \times 10^{-11} \text{ F} \\ C_2 &= 3 \times 10^{-12} \text{ F} \end{aligned}$$

⑤ FTS Plant System Identification

a) observe that the curve was shifted by -80 dB . so we shifted it back 80 dB , we have the resonance frequency at 10^3 with 20 dB

We have that

$$20 \log_{10} M_{pw} = 20$$

$$\Rightarrow M_{pw} = 10$$

For second order system we have that

$$M_{pw} = (2 \sqrt{1 - \zeta^2})^{-1}$$

$$\Rightarrow 10 = \frac{1}{2 \sqrt{1 - \zeta^2}} \Rightarrow \zeta = 0.05$$

(59)

$$\Rightarrow \omega_n = \frac{\omega_r}{\sqrt{1-2\zeta^2}} = \frac{10^3}{\sqrt{1-2\zeta^2}} \approx 1000$$

$$\Rightarrow T(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

now we shifted it back -80 dB.

$$\Rightarrow T(s) = \frac{10^{-4} \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} = \frac{100}{s^2 + 100s + (1000)^2}$$

We know that:

$$\frac{X(s)}{F(s)} = \frac{1}{m_1 s^2 + b_1 s + k_1} = \frac{\frac{1}{m_1}}{s^2 + \frac{b_1}{m_1} s + \frac{k_1}{m_1}} = \frac{100}{s^2 + 100s + (1000)^2}$$

$$\Rightarrow \boxed{\begin{array}{l} m_1 = 0.01 \\ b_1 = 100 \\ k_1 = 10^4 \end{array}}$$

5(b,c) Transferfunction: with delay part at high frequency

$$\frac{X(s)}{F(s)} = \frac{1}{m_1 s^2 + b_1 s + k_1} \quad \begin{array}{l} (-1.2 \times 10^{-5}) \\ \ell \end{array} = \frac{\ell}{0.01 s^2 + 100s + 10^4} \quad \begin{array}{l} (-1.2 \times 10^{-5}) \\ \ell \end{array}$$

$$\boxed{\frac{X(s)}{F(s)} = \frac{\ell^{(-1.2 \times 10^{-5})}}{0.01 s^2 + 100s + 10^4}}$$

(6d)

Plot the bode plot when the system is uncompensator, we saw that the phase was 200° which is unstable. now we designed a stable system with desirable phase margin by choosing $PM = 35^\circ$ at $\omega_g = 10^4$

$$\Rightarrow \phi_m = 35 - (180 - 200)$$

$$\Rightarrow \phi_m = 55^\circ \Rightarrow \alpha = \frac{1 + \sin \phi_m}{1 - \sin \phi_m} = 10.1$$

$$\Rightarrow T = \frac{1}{\omega_g \sqrt{\alpha}} = 3.15 \times 10^{-5}$$

So we was gonna use lead compensator to add more positive phase

$$\Rightarrow C_{lead} = \frac{1 + \alpha TS}{\alpha + TS} = \frac{1 + 3.15 \times 10^{-4} S}{10.1 + 3.15 \times 10^{-4} S}$$

Now we use ^acontroller to reduce the error of step input with K_i so we can increase or decrease phase margin \Rightarrow It had to increase or decrease overshoot and sensitivity.

$$\Rightarrow C_{mech} = -K_b \left(1 + \frac{K_i}{S} \right) \left(\frac{1 + 3.15 \times 10^{-4} S}{10.1 + 3.15 \times 10^{-4} S} \right)$$

$$\text{where } K_i = \frac{10^4}{5} = 0.2 \times 10^4$$

$$K_b = 2$$


$$\Rightarrow C_{mech} = -2 \left(1 + \frac{0.2 \times 10^4}{S} \right) \left(\frac{1 + 3.15 \times 10^{-4} S}{10.1 + 3.15 \times 10^{-4} S} \right)$$



(6c) Yes, when we decrease K_b the overshoot will be reduced but the sensitivity will be decreasing



Hoang Tran

505182304


DC gain from Vset to Ic: -0.50

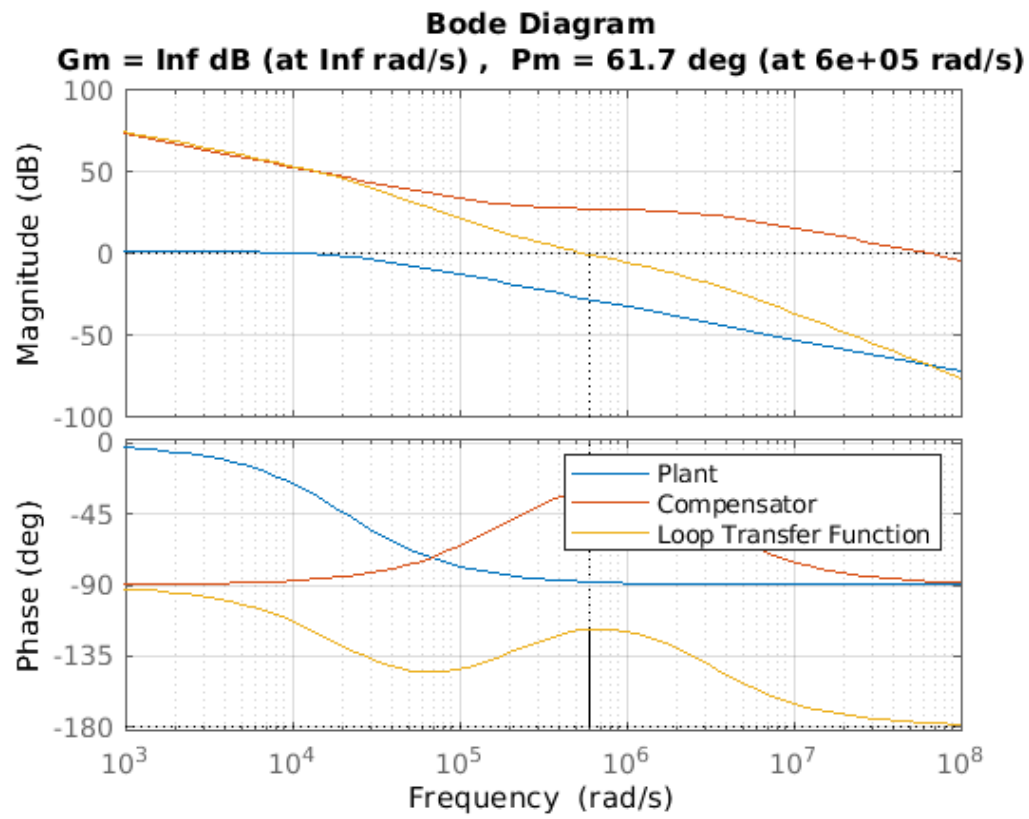

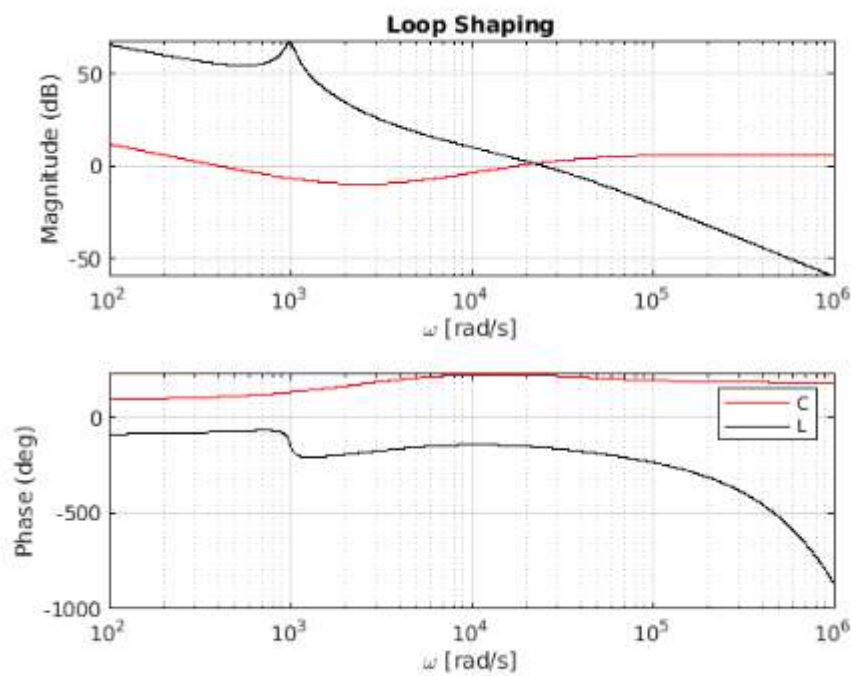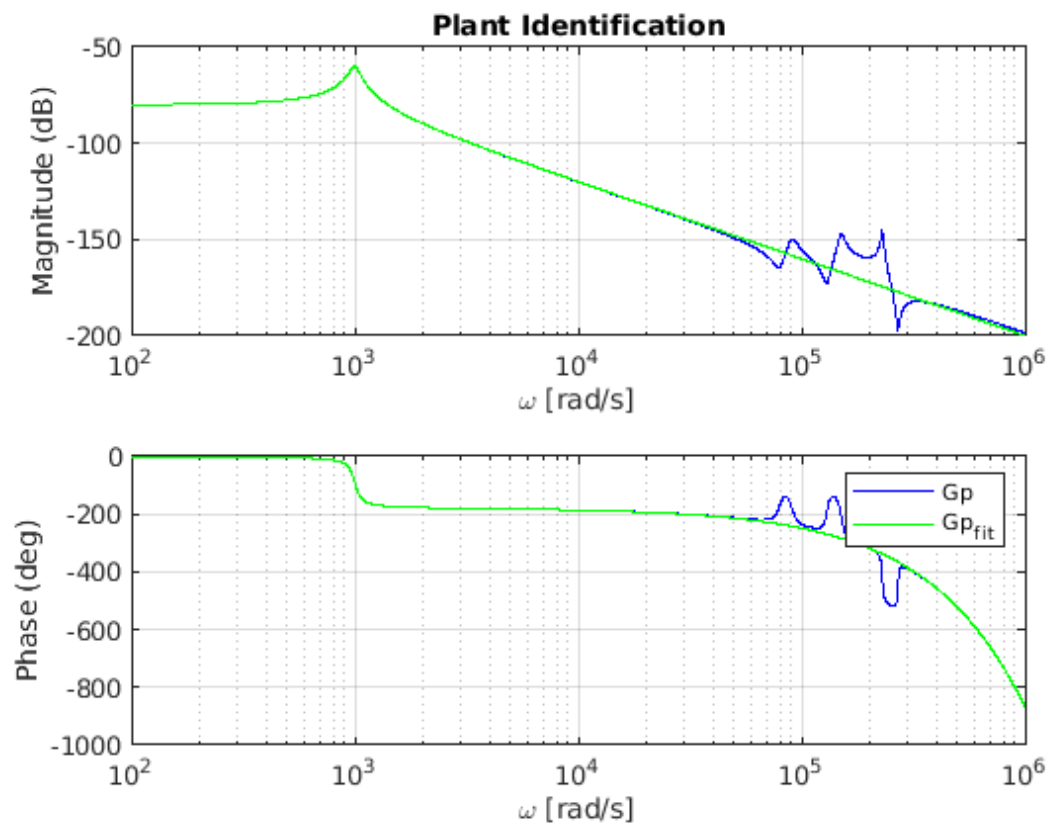


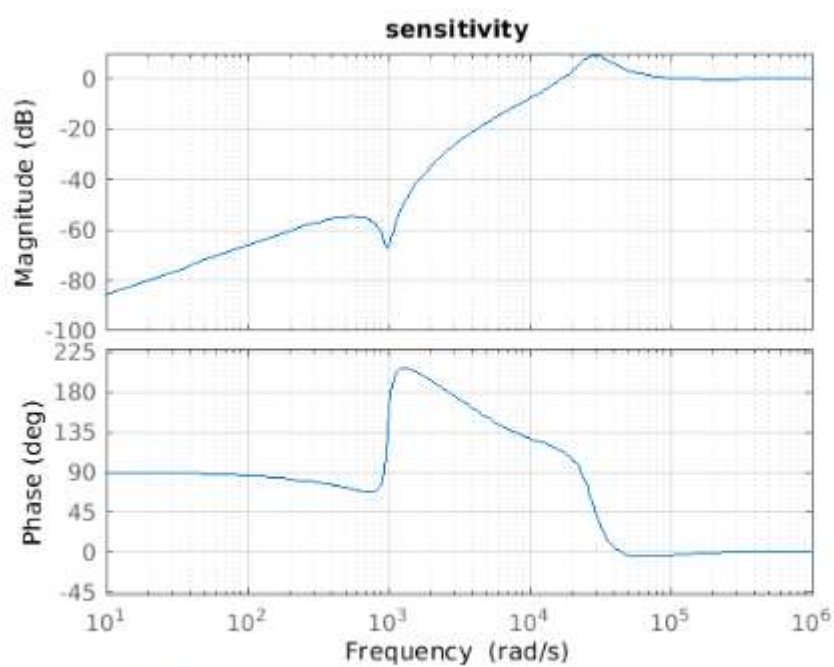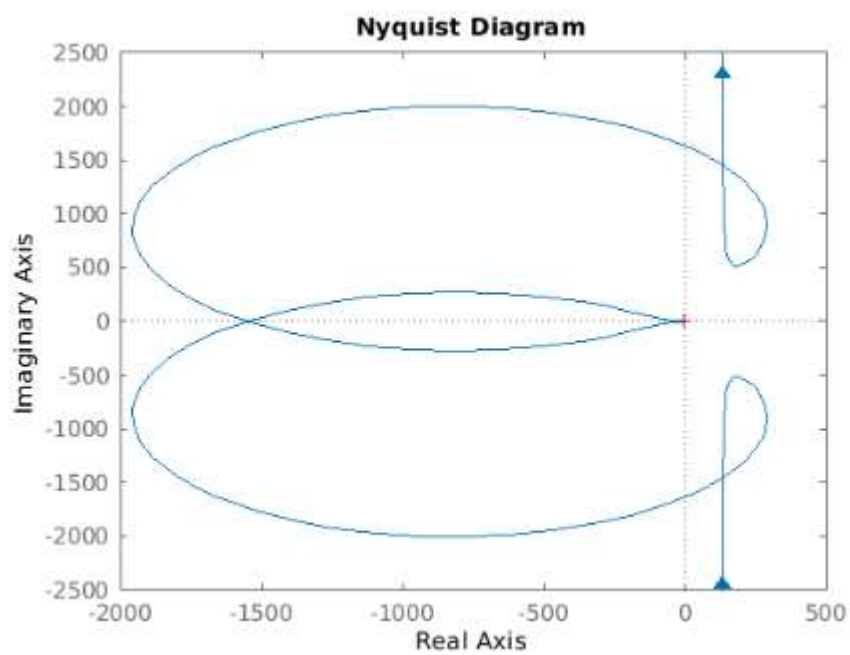


Maximum Sensitivity (dB): 9.47

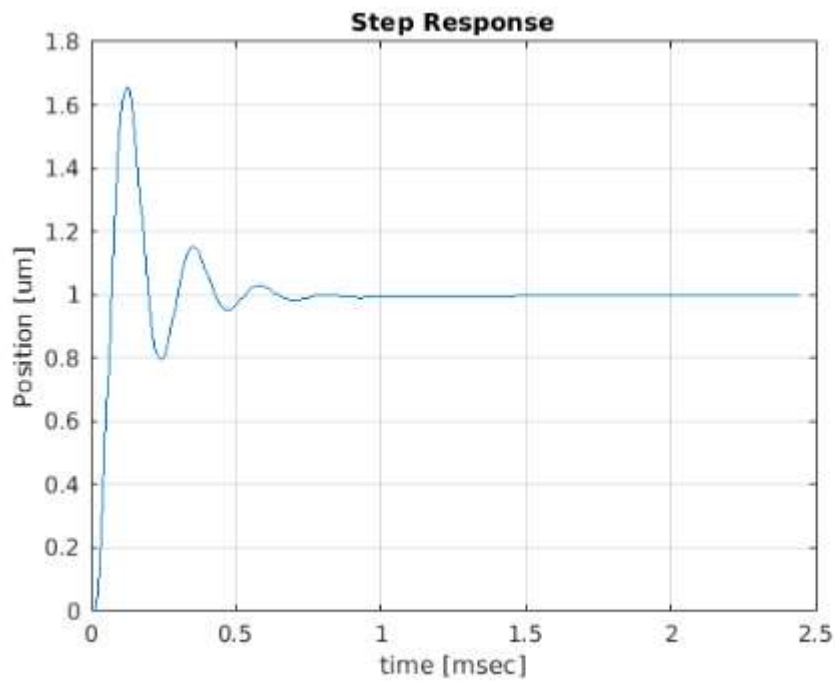

RMS SS step tracking error (nm): 0.1580

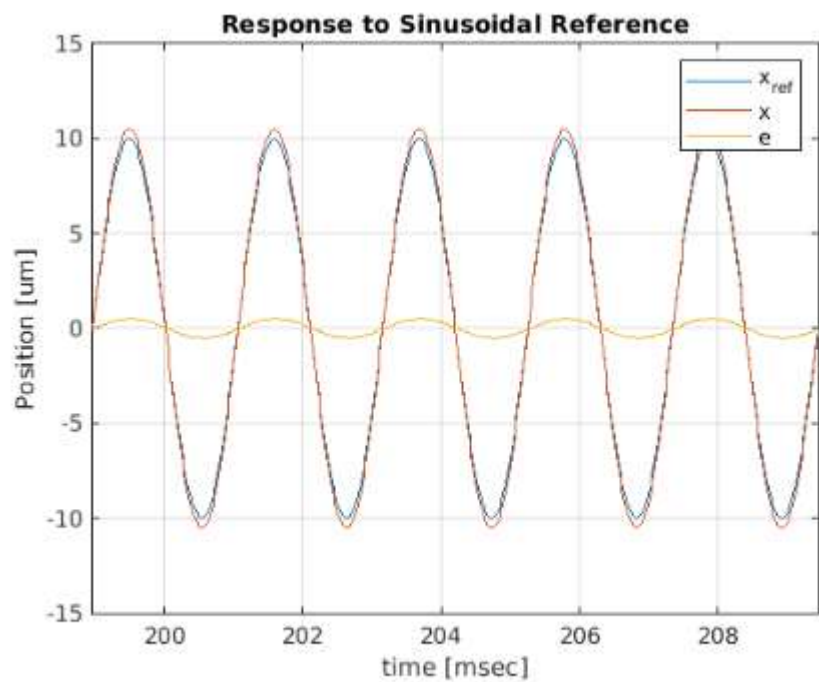

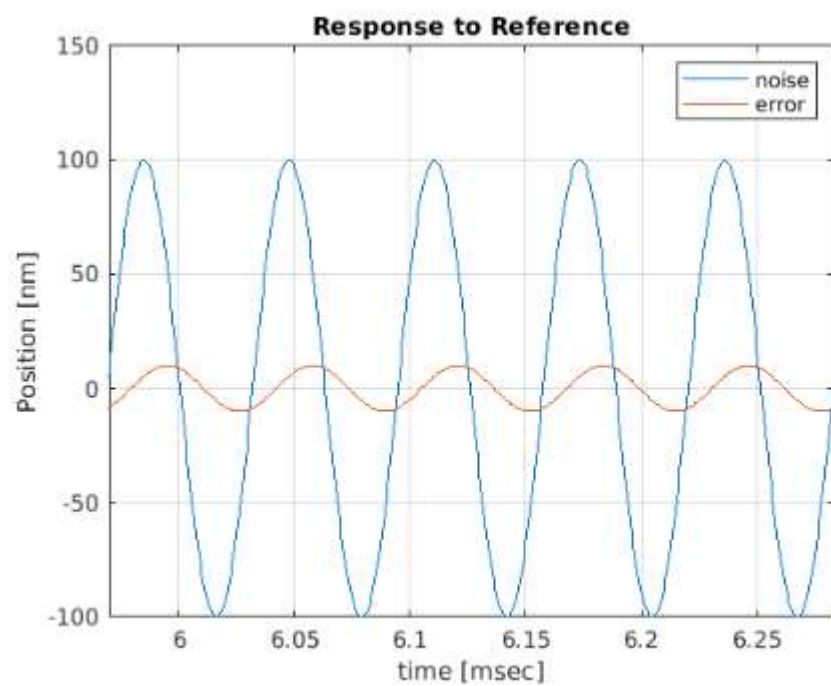RMS SS sinusoidal tracking error (μm): 0.3606



RMS SS noise error (nm): 7.1191